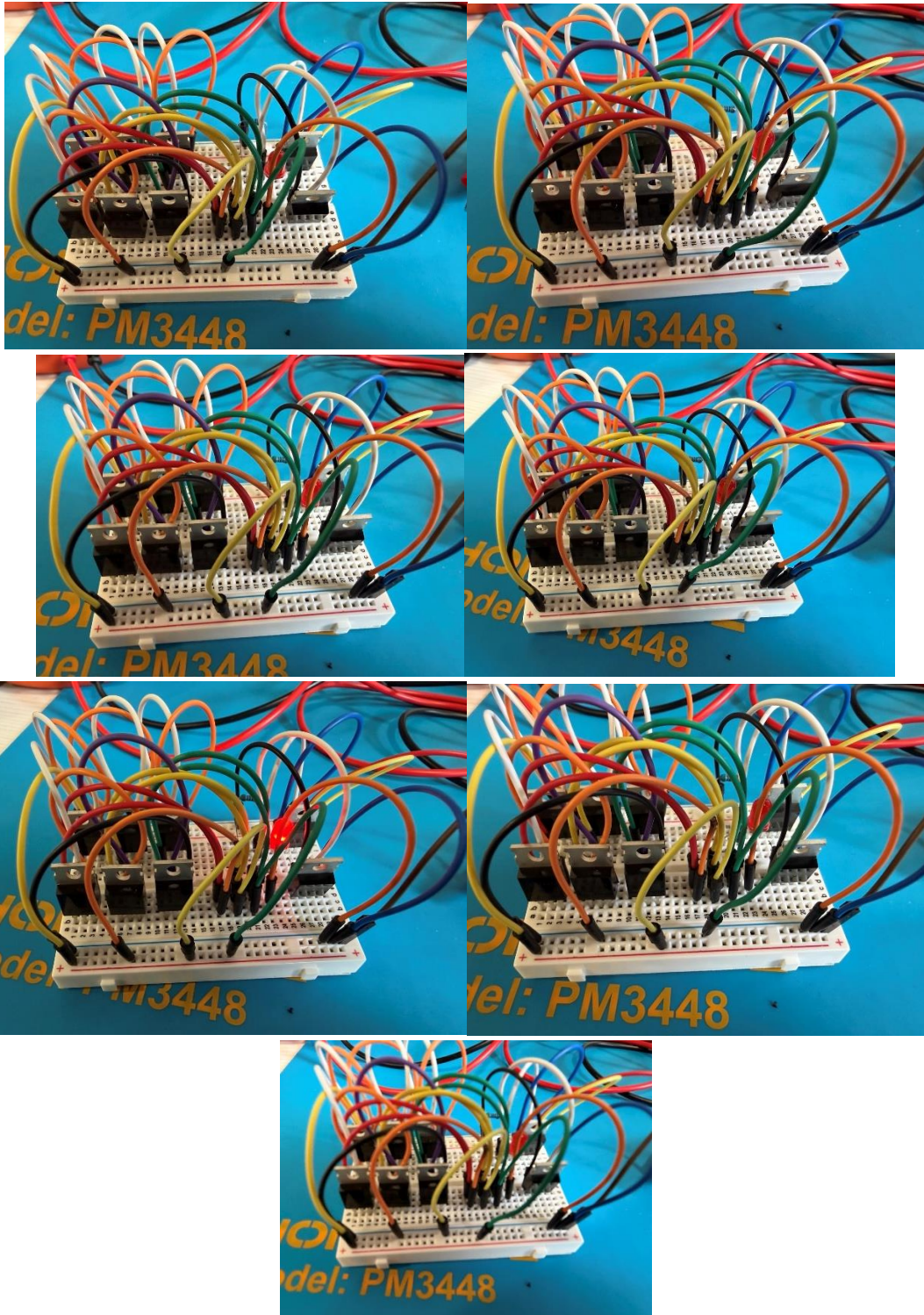


A	B	C	X
0	0	0	0
1	0	0	0
0	1	0	0
0	0	1	0
1	1	0	0
0	1	1	0
1	0	1	0
1	1	1	1


Real-life assemblies with different input cases

Orange – Yellow – Green jumper wires as input pins



In this particular circuit PMOS are connected in parallel and NMOS is series. The circuit is 3-input NAND circuit connected to Inverter MOSFET circuit's gate. NAND gives logical output 0 only when all inputs are 1, and the inverter flips that 1 to 0, hence the output becomes 1 only when all 3 inputs are 1.

Step 2: 3-input OR

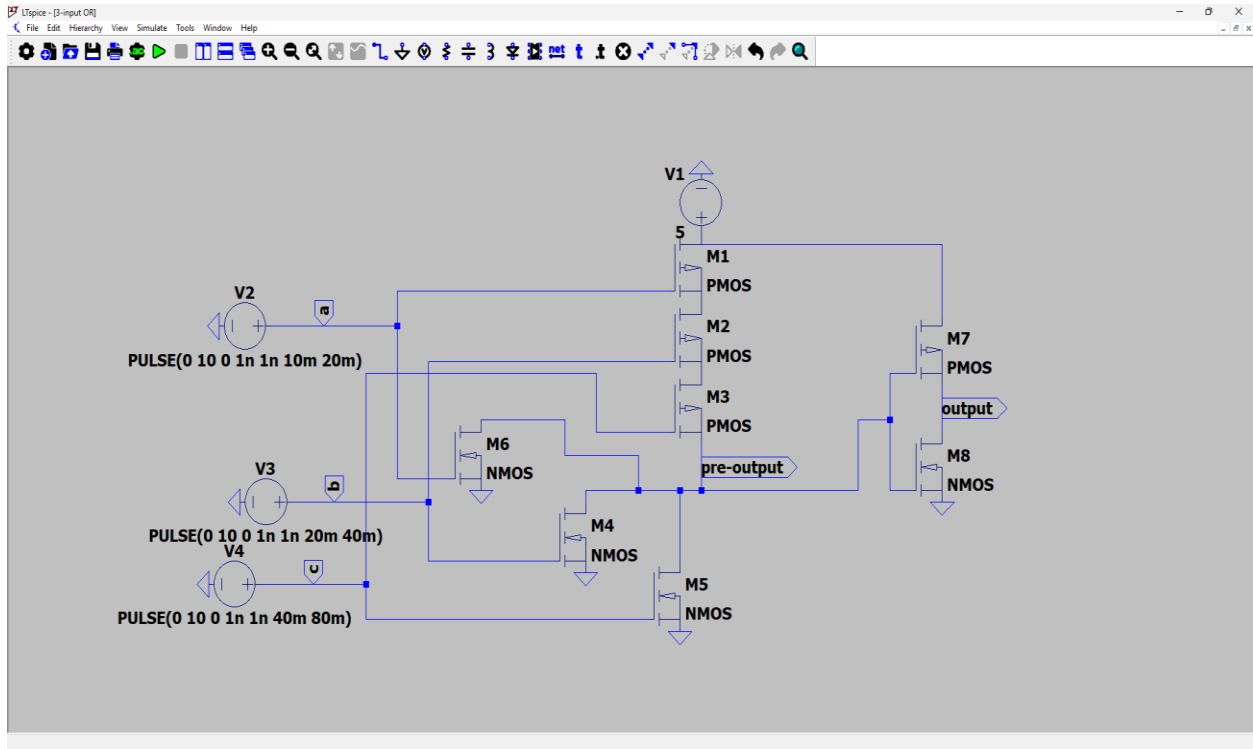


Truth Table

A	B	C	X
0	0	0	0
1	0	0	1
0	1	0	1
0	0	1	1
1	1	0	1
0	1	1	1
1	0	1	1
1	1	1	1

Real-life assemblies with different input cases

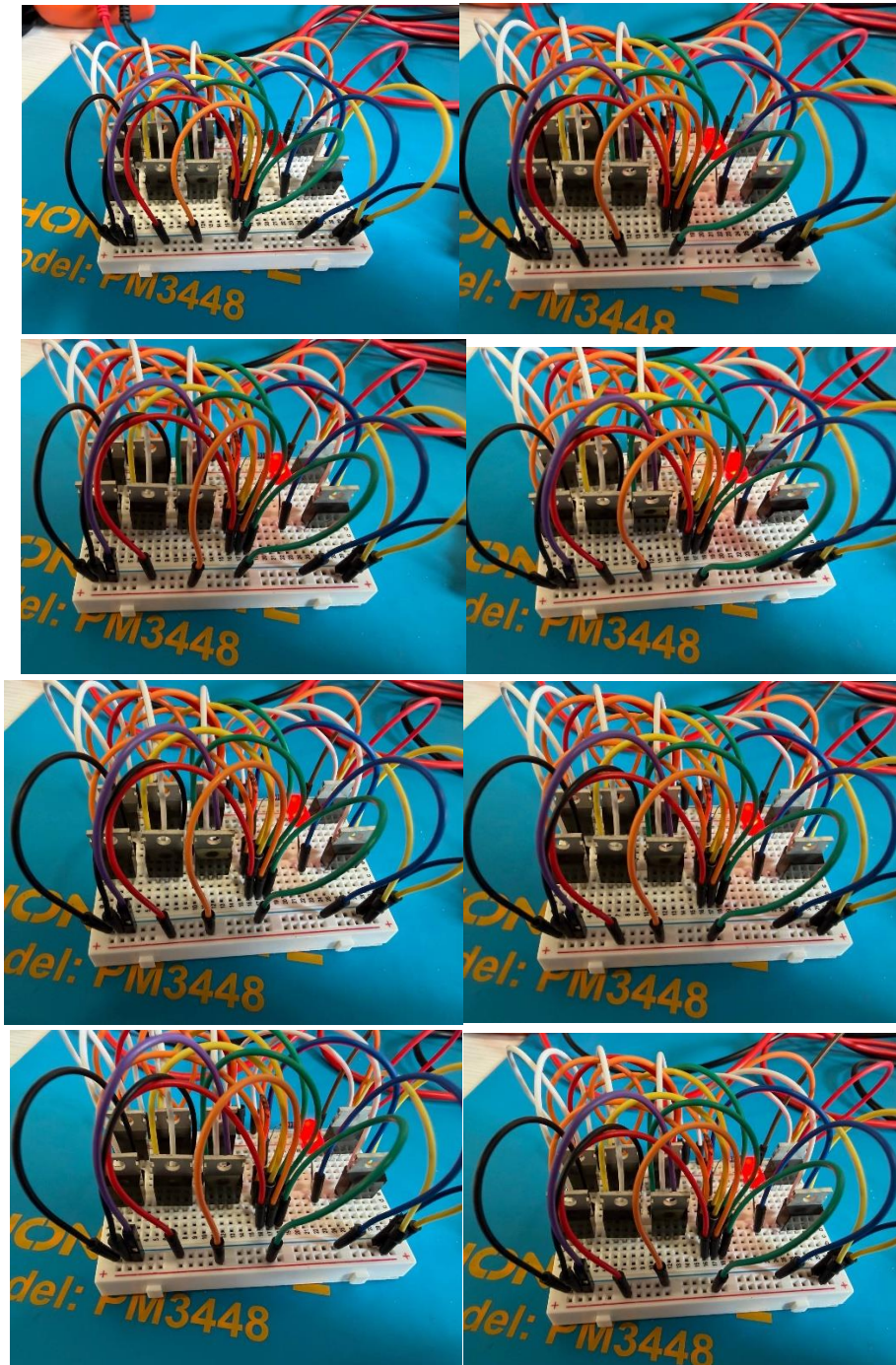Red – Yellow – Green jumper wires as input pins



In this particular circuit PMOS are connected in series and NMOS in parallel. The circuit is 3-input NOR circuit connected to Inverter MOSFET circuit's gate. NOR gives logical output 1 only when all inputs are 0, otherwise the output is always 1. The inverter flips that 1 to 0, and 0 to 1, hence the output becomes 0 only when all 3 inputs are 0, and 1 when at least one pin is 1.