

RLC Second-Order Analysis

ENGS152 Circuits Lab

6 March 2026

Step 1: RLC Calculations

We start by finding the personal resonant frequency f_0

$$f_0 = (\textit{surname length} \times \textit{name length})^2$$

Name length = 5 **Ashot**

Surname length = 10 **Nahapetyan**

$$f_0 = (5 \times 10)^2 = 2500 \text{ Hz}$$

Allowed 5% range: $2500 \pm 0.05(2500) = 2500 \pm 125 \Rightarrow [2375, 2625] \text{ Hz}$

Let $C = 0.22\mu\text{F}$ and $L = 20\text{mH}$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \approx 2399.4 \text{ HZ}, \text{ the value is within 5\% uncertainty.}$$

Quality factor is 10 ± 0.5 :

Let $R = 33 \Omega$:


$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \approx 9.14, \text{ the value falls in the range of quality factor } Q.$$

Hence:


$C = 0.22\mu\text{F}$, $L = 20\text{mH}$, $R = 33 \Omega$, $Q = 9.14$

Step 2: Circuit Design

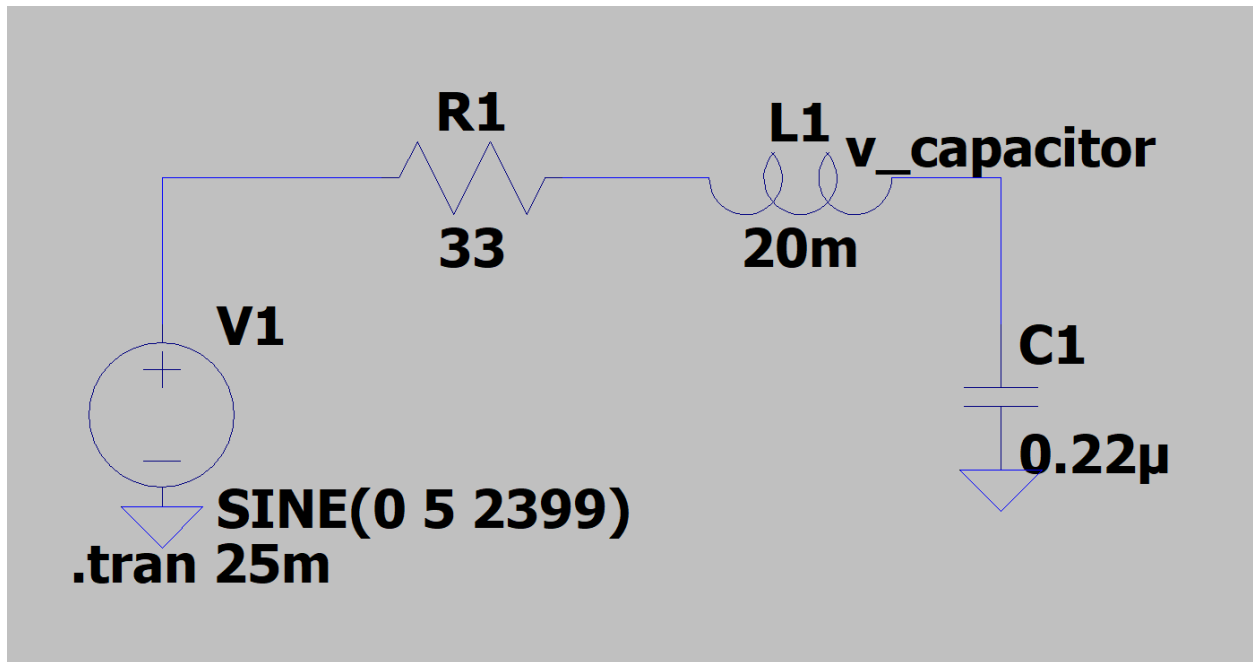First, we are asked to build the RLC circuit in LTspice using the calculated values.



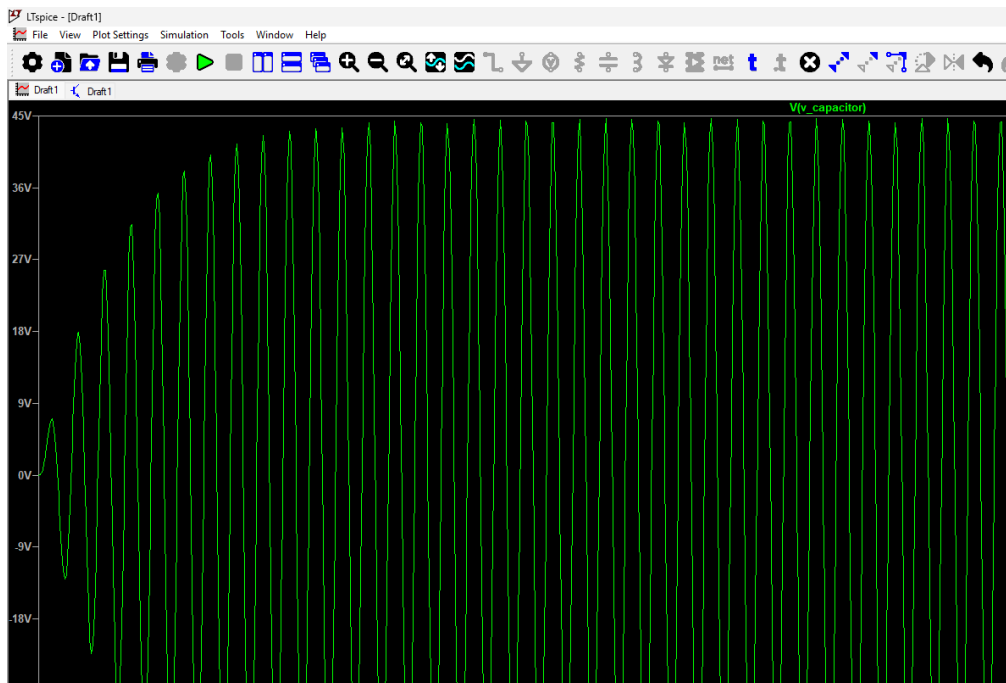After setting up the voltage source a sine wave with amplitude of 5V and frequency of 2399Hz and running the simulation, it is visible that the voltage on the capacitor reaches value of $V_C \approx 45V$




$V_c = \frac{V_{in}}{(1-1^2)^2 + \frac{1}{Q}} = V_{in} \times Q = 9.14 * 5V \approx \mathbf{45.7 V}$ (This is what happened to the voltage on the capacitor at the resonant frequency) It got amplified by the quality factor.

Bandwidth:


$B = \frac{R}{2\pi L} = \frac{33}{2\pi \times 20 \times 10^{-3}} = 262.6 \text{ Hz}$ **Bandwidth.** Below you can see the bandwidth edge frequencies.

$$f_1 = 2399 - \frac{B}{2} = 2267.7 \text{ Hz} \quad f_2 = 2399 + \frac{B}{2} = 2530.3 \text{ Hz}$$

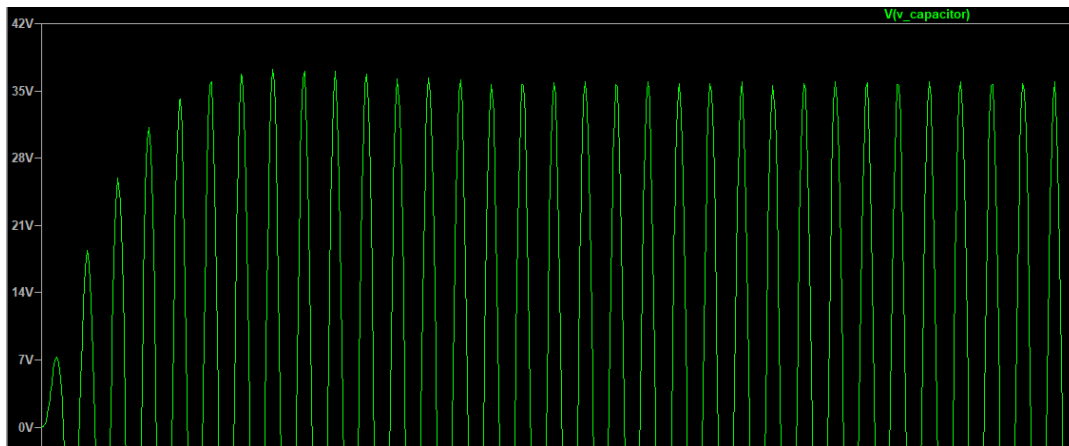At $f_1 = 2267.7 \text{ Hz}$ Peak to Peak voltage appears to be 38 V.



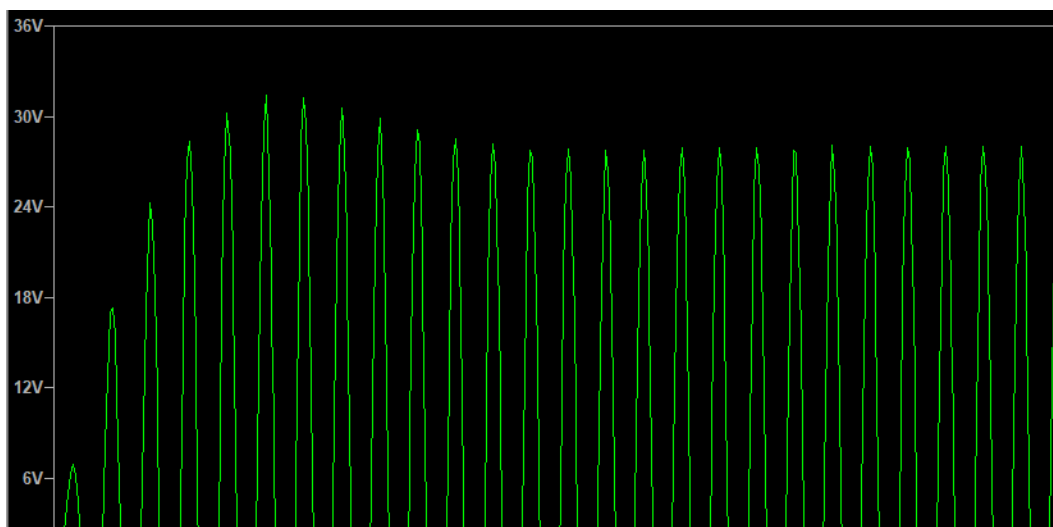At $f_2 = 2530.3 \text{ Hz}$ Peak to Peak voltage appears to be 32 V.



Lastly, we are asked to find a frequency at which the output voltage is the same as the input voltage.

$$\frac{V_c}{V_{in}} = 1$$

$$1 = \frac{1}{\left(1 - \left(\frac{f}{f_0}\right)^2\right)^2 + \left(\frac{f}{f_0 Q}\right)^2}$$

After simplifying and substituting known values we get that $f \approx \mathbf{3380\ Hz} > 2399\ Hz$. The graph below confirms it.

