

Ohm's Law and Combination of Resistors

ENGS121 Electricity & Magnetism Lab

18th September, 2025

Introduction

Resistors are used to control the current and voltage distribution through the circuits. Those are made of a piece of pure carbon connected between two pins and are meant to have some resistance. The resistors are often connected in parallel or in series, and have their own laws depending on how they are connected. All of the rules are a consequence of the law of conservation of charge and Ohm's law. The goal of the experiment is to examine those and give an evaluation.


The resistors that are used in this experiment are meant to withstand no more than 0.25W of power. In order to calculate the maximum amount of allowed voltage for the resistors Ohm's Law can be used.

$$I = \frac{V}{R}, P = U * I, P = U * \frac{U}{R} = \frac{U^2}{R} < 0.25W$$

Resistance (Ω)	100 Ω	500 Ω	1 KΩ	2 KΩ
Max. voltage (V)	5 V	11.2 V	15.8 V	22.4 V

Part 1: Voltage across the combination of resistors connected in series

Our task here is to check the validity of the formula $V = V_1 + V_2$, across the combination of resistors connected in series.

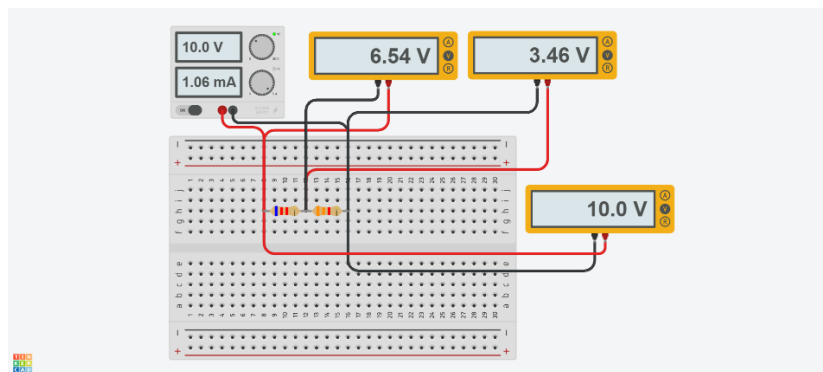

(Figure 1.1 setup of the experiment)

Instruments

Name	Quantity	Description
Breadboard	1	Board meant for connecting electrical component
Jumper Wires	-	Male-Male interface
Resistors	-	Kit of resistors with various resistances
Voltmeter	1	Meant for measuring the voltage across the circuit
Power Supply 15V	1pc	Imitates power through the circuit

Variables

Variable	Type
R_1	Parameter
R_2	Parameter
V_1	Measured
V_2	Measured
V_{All}	Control
$V_1 + V_2$	Derived

Procedure

- 1) Connect the resistors in series
- 2) Measure the resistances by Ohmmeter
- 3) Measure the voltage across R_1 , then across R_2 , lastly through both


Recorded Data

R1 (fixed)	R2 (fixed)	V1	V2	V all	V1+V2
6.17	3.26	3.63	6.86	10.49	10.49
		3.05	5.77	8.84	8.82
		2.9	5.48	8.39	8.38
		2.49	4.73	7.24	7.22
		2.26	4.26	6.56	6.52
		1.42	2.69	4.12	4.11
		1.96	3.71	5.67	5.67

Errors

<i>Description</i>	<i>Type</i>	<i>Possible Solution</i>
Power Supply Output inaccuracy	Systematic	Don't trust the power supply information screen output, record the data measured by voltmeter instead
Breadboard Wiring Resistances	Systematic	These resistances in breadboard pins are often so small that it is not worth taking into account
Current Fluctuations	Random	Hold the multi meter pins straight until a solid reading appears

Plot

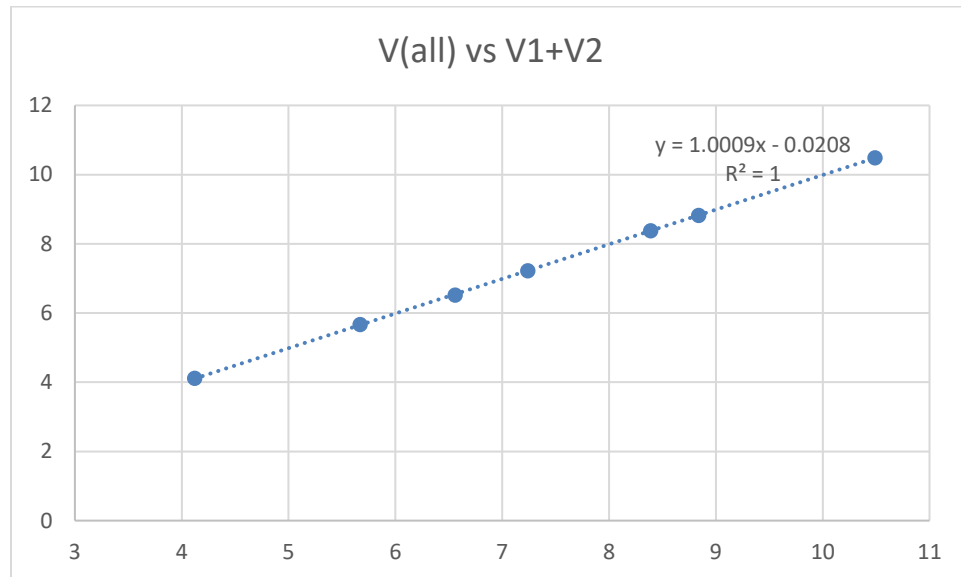


(Figure 1.5 Chi Square for the first 210 rolls.)

Evaluation and Conclusion

As we can see there is a stronger linear regression between variables V all and V1 + V2. Moreover, the slope of the trendline appears to be 1, which shows a direct linkage between two sets of variables. Hence the statement $V = V1 + V2$ is reasonable to be true.

R1	R2	V1	V2	Vall (fixed 10.11V)	V1 + V2
3.261	6.17	3.49	6.6	10.11	10.09
6.069	6.17	5.02	5.1	10.11	10.11
2.156	6.17	2.62	7.49	10.11	10.11
3.304	3.26	5.09	5.02	10.11	10.12
2.157	3.26	4.03	6.09	10.11	10.12
2.157	3.29	4.01	6.1	10.11	10.11

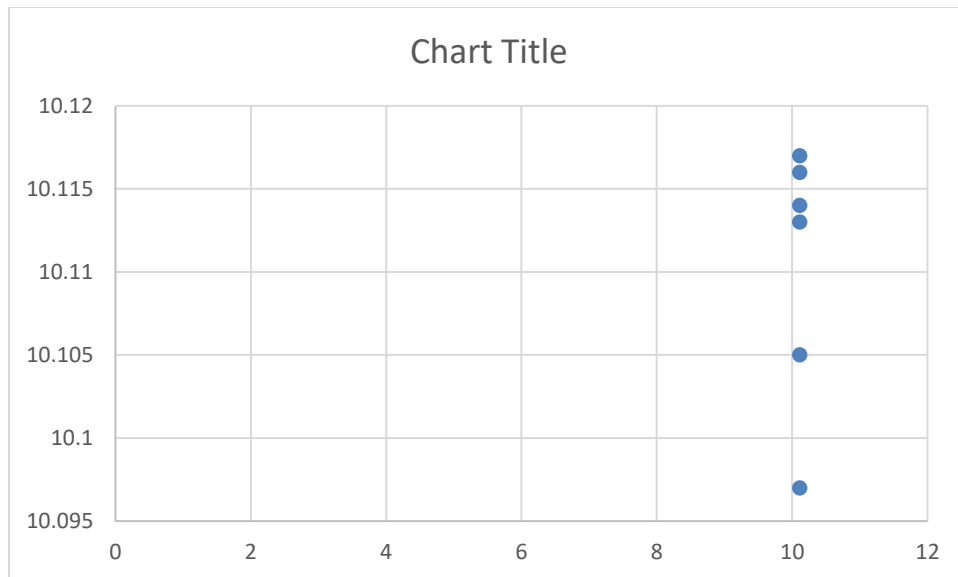

Since the plot of this case does not explain too much about the linkage between V all and V1 + V2, some other approach has to be used to evaluate the results. One way to do that is by computing the differences.

$$\mu = 10.11 \text{ V}$$

$$\sigma = 0.01 \text{ V}$$

The average value of V1 + V2 is exactly equal to the value of Vall

$$\Delta V = 0$$

The relative error is negligible, implies that V1 + V2 => Vall is valid.

Part 2: Ohm's Law

Check if the current through the circuit is proportional to across the resistor.

Errors


<i>Description</i>	<i>Type</i>	<i>Possible Solution</i>
Power Supply Output inaccuracy	Systematic	Don't trust the power supply information screen output, record the data measured by voltmeter instead
Breadboard Wiring Resistances	Systematic	These resistances in breadboard pins are often so small that it is not worth taking it into account
Current Fluctuations	Random	Hold the multi meter pins straight until a solid reading appears
Resistor Factory Imperfections	Systematic	-

Variable	Type
R_1	Parameter
R_2	Parameter
V_1	Measured
V_2	Measured
V_{All}	Control
V_1/R_1	Derived
V_2/R_2	Derived

Recorded Data


R_1	R_2	V_1	V_2	V_{all}	V_1/R_1	V_2/R_2
3.26	6.17	3.63	6.86	10.49	1.11	1.11
3.26	6.17	3.05	5.77	8.84	0.94	0.94

3.26	6.17	2.90	4.48	8.39	0.89	0.73
3.26	6.17	2.49	4.73	7.24	0.76	0.77
3.26	6.17	2.26	4.26	6.56	0.69	0.69
3.26	6.17	1.42	2.69	4.12	0.44	0.44
3.26	6.17	1.96	3.71	5.67	0.60	0.60
3.26	6.17	3.50	6.60	10.11	1.07	1.07
6.07	6.70	5.02	4.10	10.11	0.83	0.61
2.16	6.17	2.62	7.49	10.11	1.21	1.21
3.30	3.26	5.09	5.02	10.11	1.54	1.54
2.16	3.26	4.03	6.09	10.11	1.87	1.87
2.16	3.29	4.01	6.10	10.11	1.86	1.85

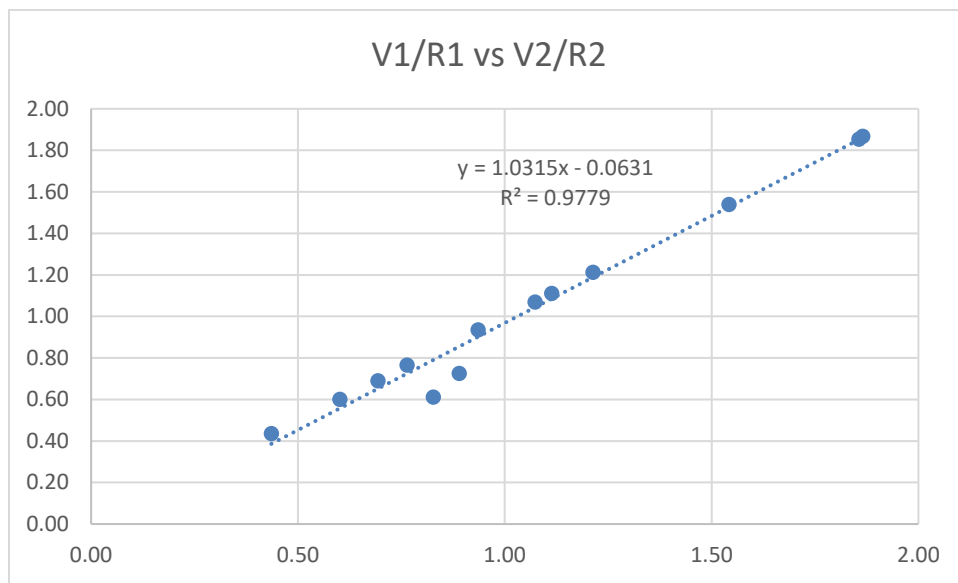

As we can see $R^2 \approx 0.978$, which shows a very strong linear relationship, so $V1/R1 \approx V2/R2$ indicating that the current is proportional to voltage as Ohm's law predicts. There are some minor deviations which are likely due to experimental errors, but overall, the validity of Ohm's Law is supported.

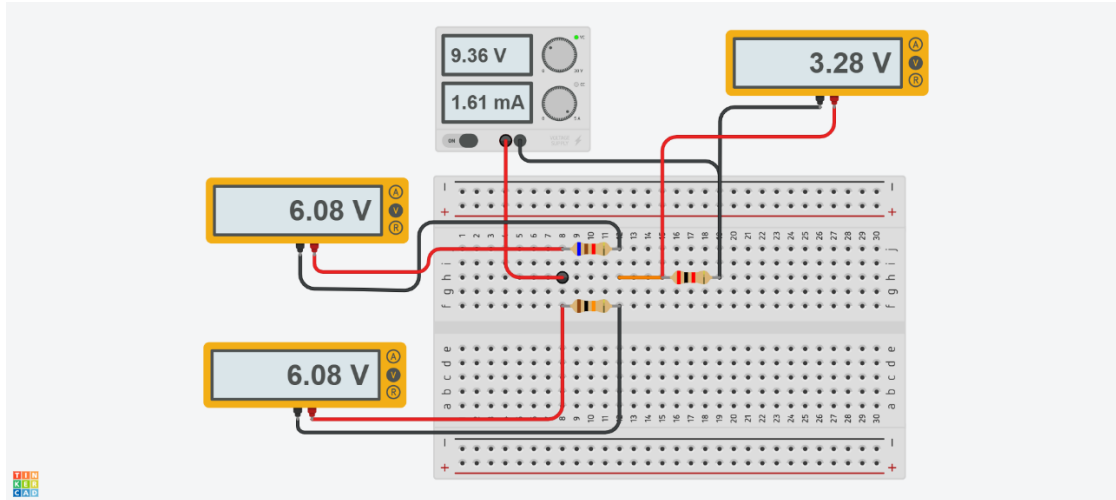Part 3: Testing the junction rule for parallel connection



According to the conservation law of charge sum of the currents through each resistor must be equal to the total current through the combination.

Variable	Type
R_1	Control
R_2	Control
R_3	Control
V_1	Measured
V_2	Measured
V_3	Measured
V_{All}	Fixed
$V_1/R_1 + V_2/R_2$	Derived
V_3/R_3	Derived


$$V_{All} = 9.36 \text{ V (fixed)}$$

Errors

Description	Type	Possible Solution
Power Supply Output inaccuracy	Systematic	Don't trust the power supply information screen output, record the data measured by voltmeter instead
Breadboard Wiring Resistances	Systematic	These resistances in breadboard pins are often

		so small that it is not worth taking it into account
Current Fluctuations	Random	Hold the multi meter pins straight until a solid reading appears
Resistor Factory Imperfections	Systematic	-

R1	R2	R3	V1	V2	V3	$\frac{V_1}{R_1} + \frac{V_2}{R_2}$	$\frac{V_3}{R_3}$
6.09	9.97	2.04	6.09	6.09	3.29	1.61	1.61
2.04	9.97	6.09	2.04	2.04	7.33	1.20	1.20
2.04	6.09	9.97	1.24	1.24	8.13	0.81	0.82
2.04	6.09	2.14	3.91	3.90	5.47	2.56	2.56
7.34	3.30	1.97	5.02	5.02	4.36	2.21	2.21
2.14	1.97	3.30	2.22	2.22	7.14	2.16	2.16
2.14	1.97	7.34	1.27	1.25	8.21	1.23	1.12

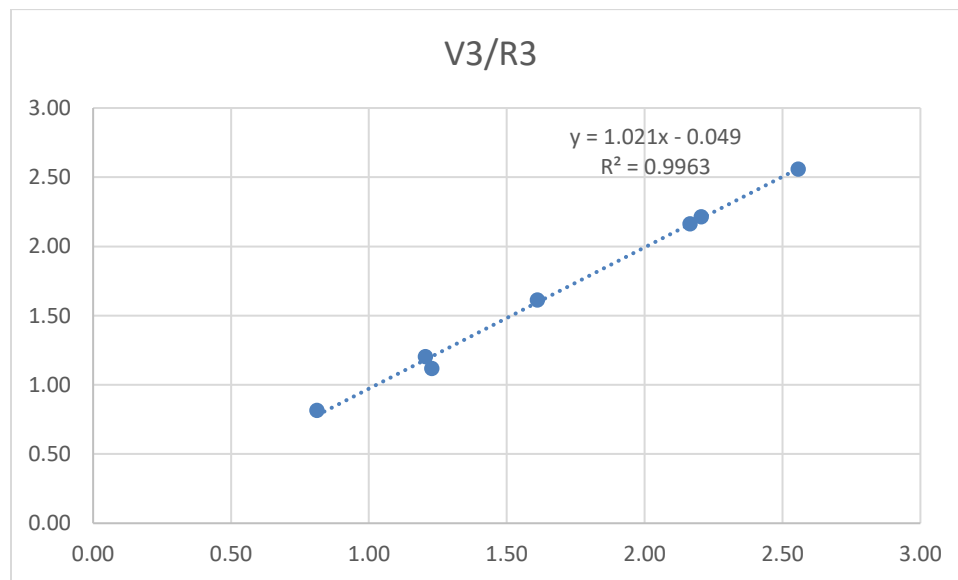

As we can see $R^2 \approx 0.996$, which shows a very strong linear relationship, so

$\frac{V_1}{R_1} + \frac{V_2}{R_2} \approx \frac{V_3}{R_3}$ indicating that the sum of the currents through R1 and R2 equals the current through

R3, supporting the validity of the junction rule.

